



SIMULATION OF STEADY-STATE BEHAVIOR OF SINUSOIDALLY EXCITED RLC SERIES CIRCUIT

A MATLAB APPROACH


BY: OHMEGA EAGLES


IMAN AYAZ, THOMAS TEMPLIN, DANIEL ILOH

PROBLEM STATEMENT

- The concept of RLC circuits is learned in Physics courses at various levels. An RLC circuit is an electrical circuit containing a Resistor(R), an inductor(L) and a capacitor(C) connected in series or in parallel. They are used in radios, televisions, oscillation circuits etc. The goal of group is to create an application that provides the output graph and phasor diagram for an RLC circuit with a given input of frequency and amplitude. We are making it as an educational tool and as a visualization to demonstrate how RLC circuits work. It will help in understanding the mathematical equations associated with RLC circuits. The phasor diagram and the graph show the expected relationship between the amplitude and the phase of the resistor, capacitor and inductor.

APPROACH

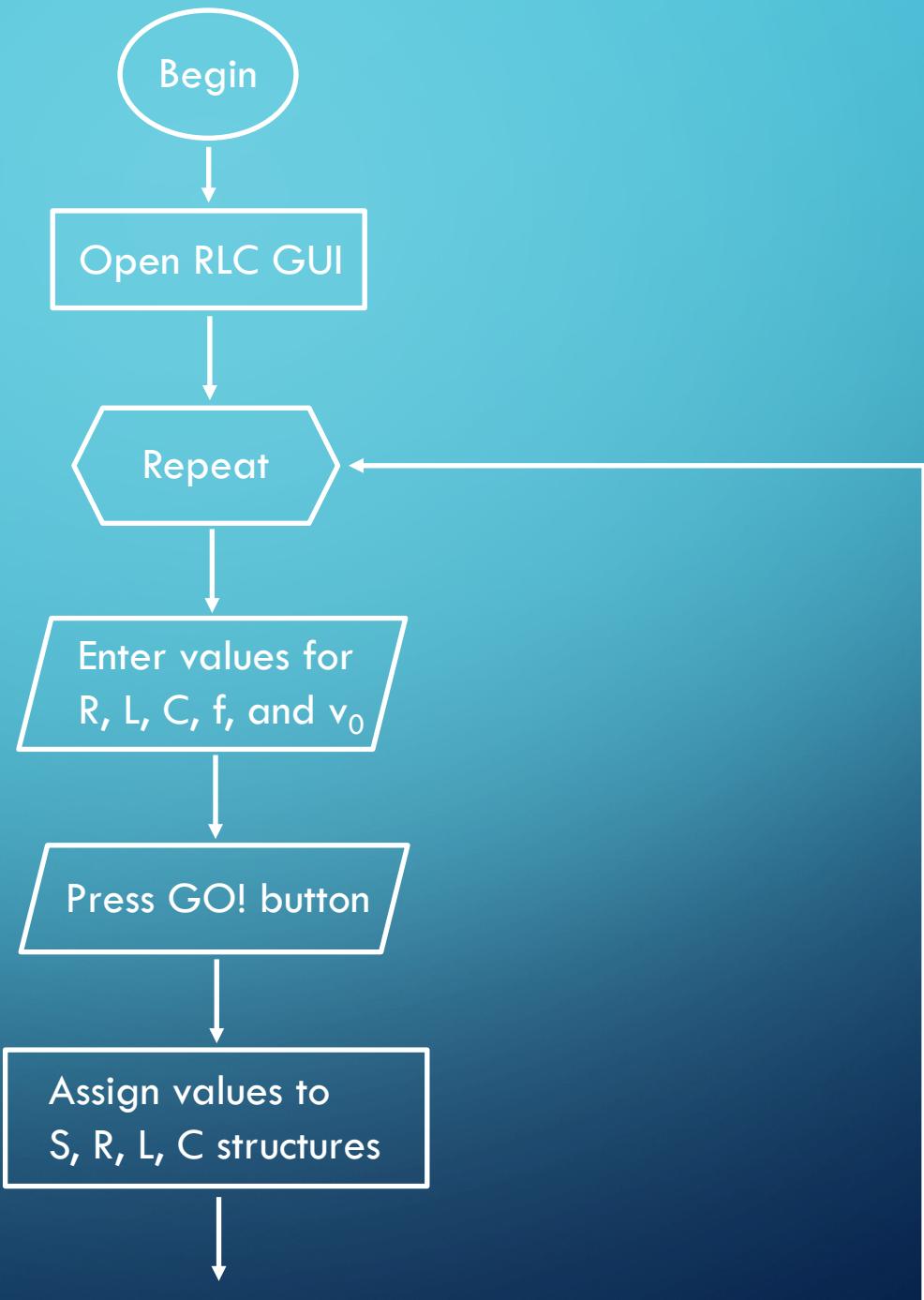

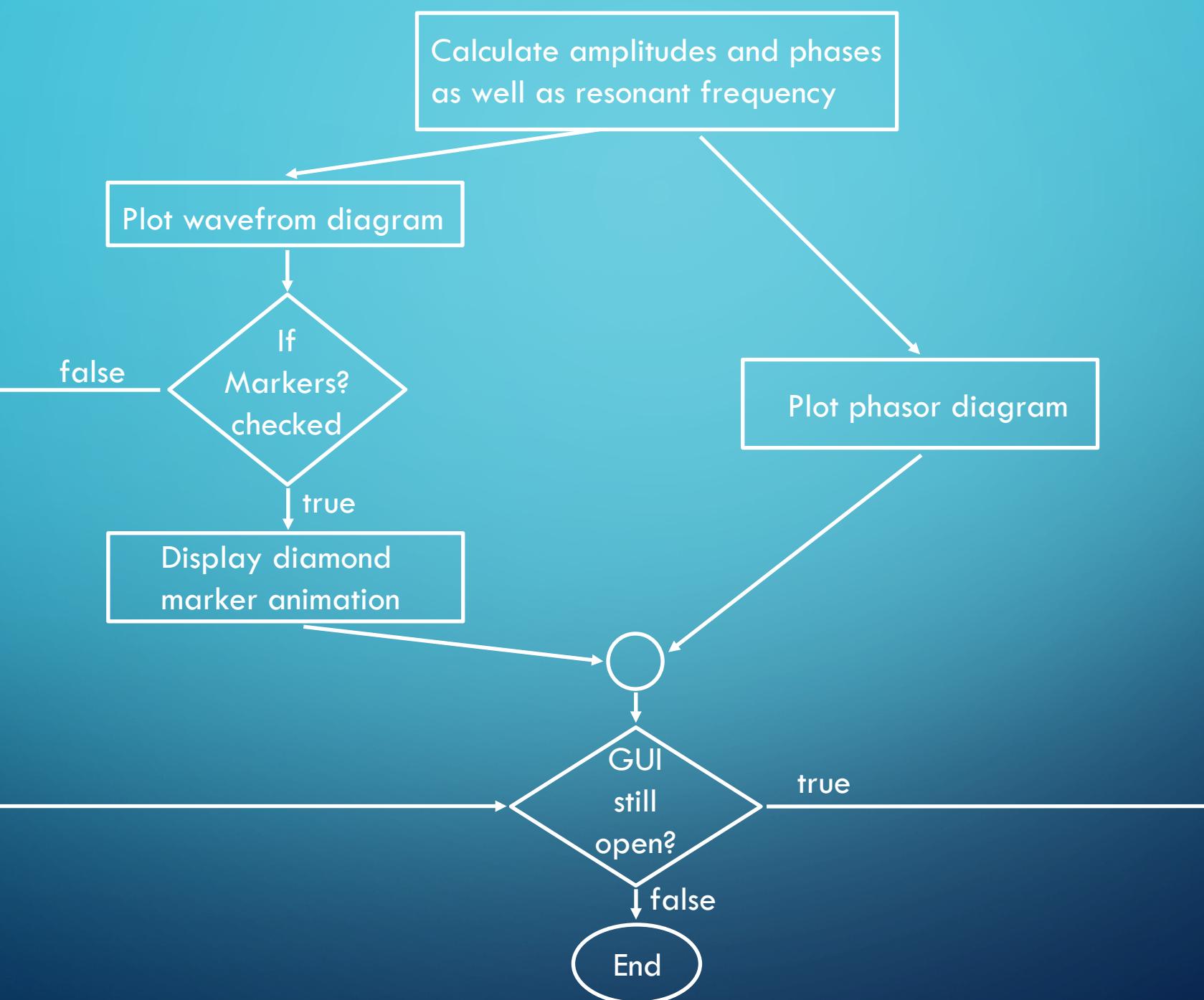

MATLAB CODE

- For loop (marker animation)
- String manipulation [`str2double(...)`, `strcat(...)`]
- Plots (GUI, waveform and phasor diagrams)
- Functions (10 regular + 18 GUI functions)
- Structures (one each for S, R, L, and C)

```
function amplitude = calculate_amplitude(w_in, v0, R, L, C, type)
% Calculates and returns magnitude of waveform of circuit element
%{

    Formal parameters:
    w_in: angular frequency of voltage source (rad/s)
    v0: amplitude of voltage source (V)
    R: series resistance (ohm)
    L: series inductance (H)
    C: series capacitance (F)
    type: a passive circuit element ('R', 'L', or 'C')

}

den = sqrt((1-w_in^2*L*C)^2 + (w_in*R*C)^2);      % denominator of expression
switch type
    case 'R'    % resistor
        amplitude = v0*w_in*R*C/den;
    case 'L'    % inductor
        amplitude = v0*w_in^2*L*C/den;
    case 'C'    % capacitor
        amplitude = v0/den;
end
end
```

```
% Toggle for animation
if anim_flag

    % Assignment of plot handles for markers
    S.p = assign_plots(t, S.amp, S.amp, 0, 'k');
    R.p = assign_plots(t, S.amp, R.amp, R.phi, 'r');
    L.p = assign_plots(t, S.amp, L.amp, L.phi, 'g');
    C.p = assign_plots(t, S.amp, C.amp, C.phi, 'b');

    % Add moving markers
    len_t = length(t);
    for k = 2:4:len_t
        animate_waveform(S.p, t, k, S.omg, S.amp, 0)          % voltage source
        animate_waveform(R.p, t, k, S.omg, R.amp, R.phi)      % resistor
        animate_waveform(L.p, t, k, S.omg, L.amp, L.phi)      % inductor
        animate_waveform(C.p, t, k, S.omg, C.amp, C.phi)      % capacitor
    end
```

SOME FUNCTIONS USED:

- `imread` (for matlab to read the code of external images and load them into the folder)
- `imshow` (to display the image)
- `axes` (to place the image on certain axes)

```
guidata(hObject, handles);  
theImage=imread('Copy_of_circuit.jpg'); % load circuit image  
axes(handles.Inputs); % assin axes handles  
imshow(theImage); % display image
```

```
phasorDiagram.m +  
1 function diagram = phasorDiagram(w_in, v0, R, L, C)  
2  
3 - amplitudeR = calculate_amplitude(w_in, v0, R, L, C, 'R');  
4 - amplitudeL = calculate_amplitude(w_in, v0, R, L, C, 'L');  
5 - amplitudeC = calculate_amplitude(w_in, v0, R, L, C, 'C');  
6  
7 - phaseR = calculate_phase(w_in, R, L, C, 'R');  
8 - phaseL = calculate_phase(w_in, R, L, C, 'L');  
9 - phaseC = calculate_phase(w_in, R, L, C, 'C');  
10  
11  
12 - x_start = 0;% Starting position  
13 - y_start = 0;  
14  
15 %PLOT THE AXES  
16 - angle = (0)*pi/180; % Bearing angle  
17 - [x,y] = pol2cart(angle,350);  
18 % Draw line between start and target  
19 - davinci('arrow','X',[x_start x],'Y',[y_start y],'Color'...  
     ,[0.5 0.5 0.5], 'LineWidth',1,'Head.Length',10,'Head.Width',20);  
20  
21  
22 - hold on  
23  
24 - angle = (90)*pi/180; % Bearing angle  
25 - [x,y] = pol2cart(angle,350);  
26 % Draw line between start and target  
27 - davinci('arrow','X',[x_start x],'Y',[y_start y],'Color'...  
     ,[0.5 0.5 0.5], 'LineWidth',1,'Head.Length',10,'Head.Width',20);  
28  
29  
30  
31
```

```
phasorDiagram.m x +  
46 -     [x,y] = pol2cart(angle,v0);  
47 - % Draw line between start and target  
48 - davinci('arrow','X',[x_start x],'Y',[y_start y],'Color'...  
49 -     , 'k', 'LineWidth', 2, 'Head.Length', 30, 'Head.Width', 30);  
50 -  
51 -  
52 -  
53 - %code for Vr  
54 - [x,y] = pol2cart(phaseR,amplitudeR);  
55 - % Draw line between start and target  
56 - davinci('arrow','X',[x_start x],'Y',[y_start y],'Color'...  
57 -     , 'red', 'LineWidth', 2, 'Head.Length', 30, 'Head.Width', 30);  
58 -  
59 - %code for Vl  
60 - [x,y] = pol2cart(phaseL,amplitudeL);  
61 - % Draw line between start and target  
62 - davinci('arrow','X',[x_start x],'Y',[y_start y],'Color'...  
63 -     , 'green', 'LineWidth', 2, 'Head.Length', 30, 'Head.Width', 30);  
64 -  
65 - %code for Vc  
66 - [x,y] = pol2cart(phaseC,amplitudeC);  
67 - % Draw line between start and target  
68 - davinci('arrow','X',[x_start x],'Y',[y_start y],'Color'...  
69 -     , 'blue', 'LineWidth', 2, 'Head.Length', 30, 'Head.Width', 30);  
70 -  
71 -  
72 - axis equal  
73 - axis([-v0*1.5 v0*1.5 -v0*1.5 v0*1.5])  
74 -  
75 - end  
76 -
```

FUNCTIONS USED FOR PHASOR DIAGRAM

- Pol2cart – Transform polar or cylindrical coordinates to Cartesian for plotting.
- Davinci – uses low level MATLAB graphics commands to draw midlevel shapes.
Can be used instead of plot to add more graphics.

CHALLENGES

- Showing the RLC circuit in the GUI
- Integrating both circuit codes into the GUI code

